
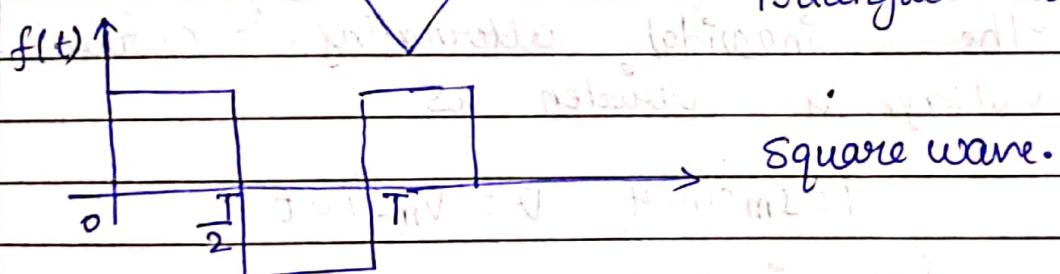
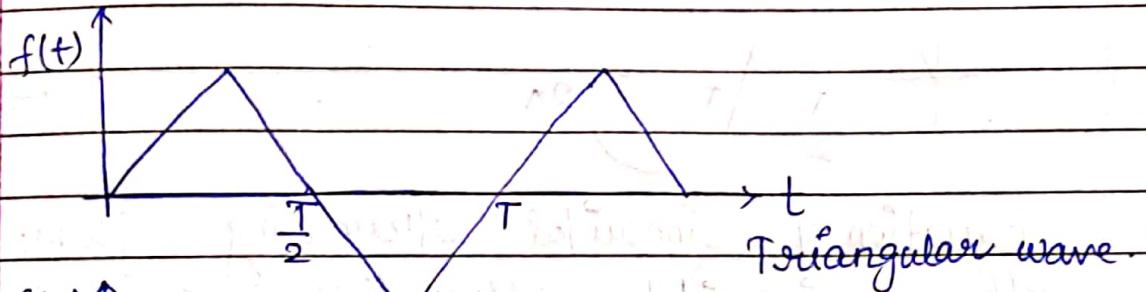


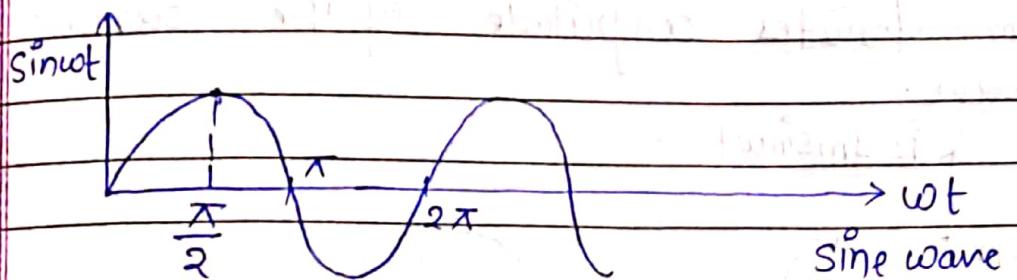* Alternating quantity:- quantity which varies periodically with time is known as Alternating quantity. It may be voltage or current. Some wave forms of Alternating quantities are



Cycle

It is the one complete set of positive and negative half cycle of any alternating quantity.

Time period:-

If it is the time required in second to complete the one cycle of any alternating quantity.

$$\text{frequency:- } f = \frac{\text{poles revolution}}{120}$$


No. of cycles per second is known as the frequency of alternating quantity.

It is the reciprocal of the time and its unit is cycle/second or Hertz (Hz) ($f = \frac{1}{T}$ in Hertz)

Amplitude-

It is the peak or maximum value of the alternating quantity in the given fig.
I_m denotes amplitude of the current wave.

$$i = I_m \sin \omega t$$

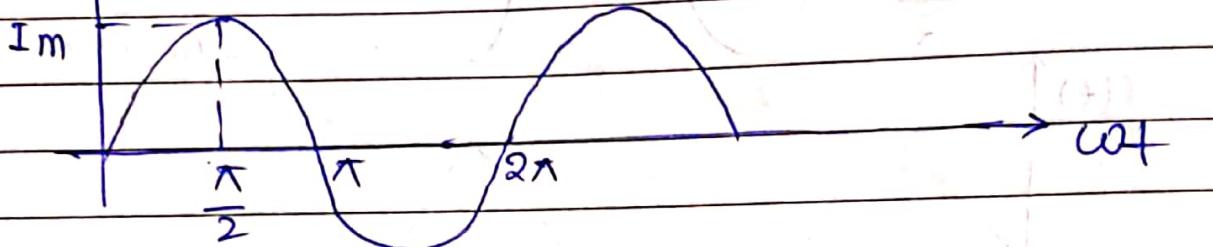

Equation of sinusoidal alternating quantity of the sinusoidal alternating current and voltage is written as -

$$i = I_m \sin \omega t \quad V = V_m \sin \omega t$$

i, v - instantaneous value of current & voltage

I_m, V_m - Maximum value / peak value.

$$\omega = 2\pi f = \frac{2\pi}{T} \quad f = \text{frequency in Hz}$$

$$- \left\{ X_L = \omega L \quad X_C = \frac{1}{\omega C} \right\}$$


Phase:-

Phase of any alternating quantity shows the position of wave at any time after it has passed through the zero position of reference.

→ Phase angle is the angle of alternating quantity w.r.t to reference position.

- Phase difference

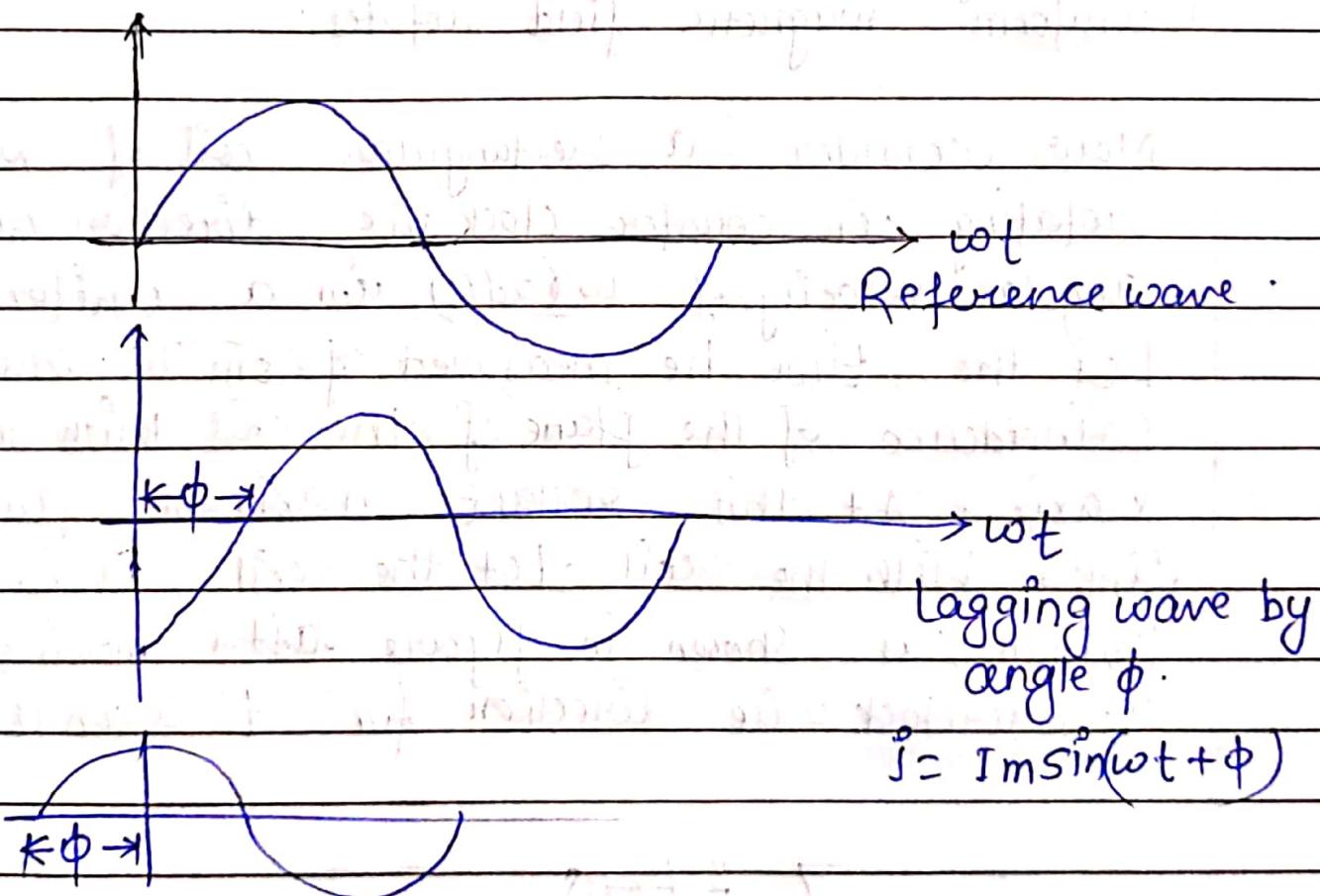When the maxima and minima of two sinusoidal alternating quantities of same frequency) are not occur at the same instant of time, then these two quantities are said to have phase difference.



- Generation of Induced Emf:-


We know that alternating Emf can be generated either by rotating a coil with in a stationary magnetic field or by rotating a magnetic field with in a stationary coil.


The emf generated in either case will be of sinusoidal wave form. The magnitude of emf generated in the coil depends upon the number of turns on the coil, the strength of magnetic field and the speed at which the coil or magnetic field rotates.

Now consider a rectangular coil of N -turns rotating in counter clockwise direction with angular velocity of ω (rad/s) in a uniform magnetic field rotates.

Now consider a rectangular coil of N -turns rotating in counter clockwise direction with angular velocity of ω (rad/s) in a uniform M.F.

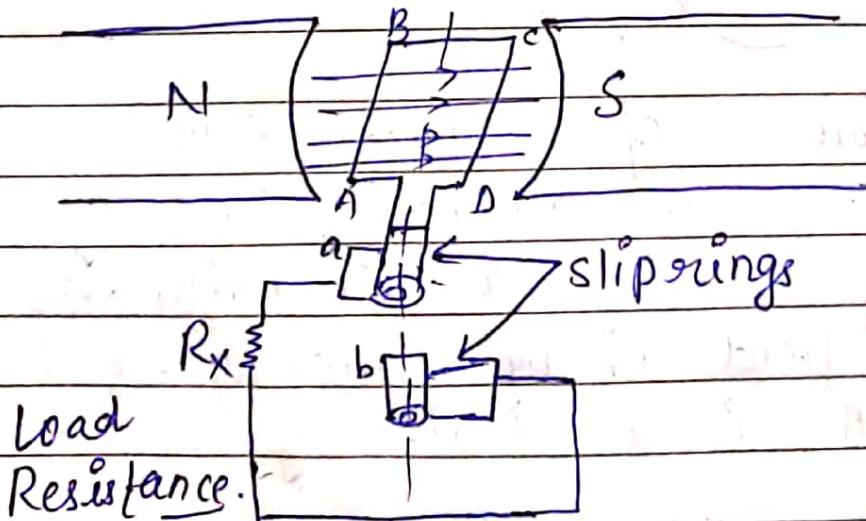Let the time be measured from the instant of coincidence of the plane of the coil with the x-axis. At this instant maximum flux (ϕ) links with the coil. Let the coil, assume the position, as shown in figure after moving in counterclockwise direction for 't' seconds



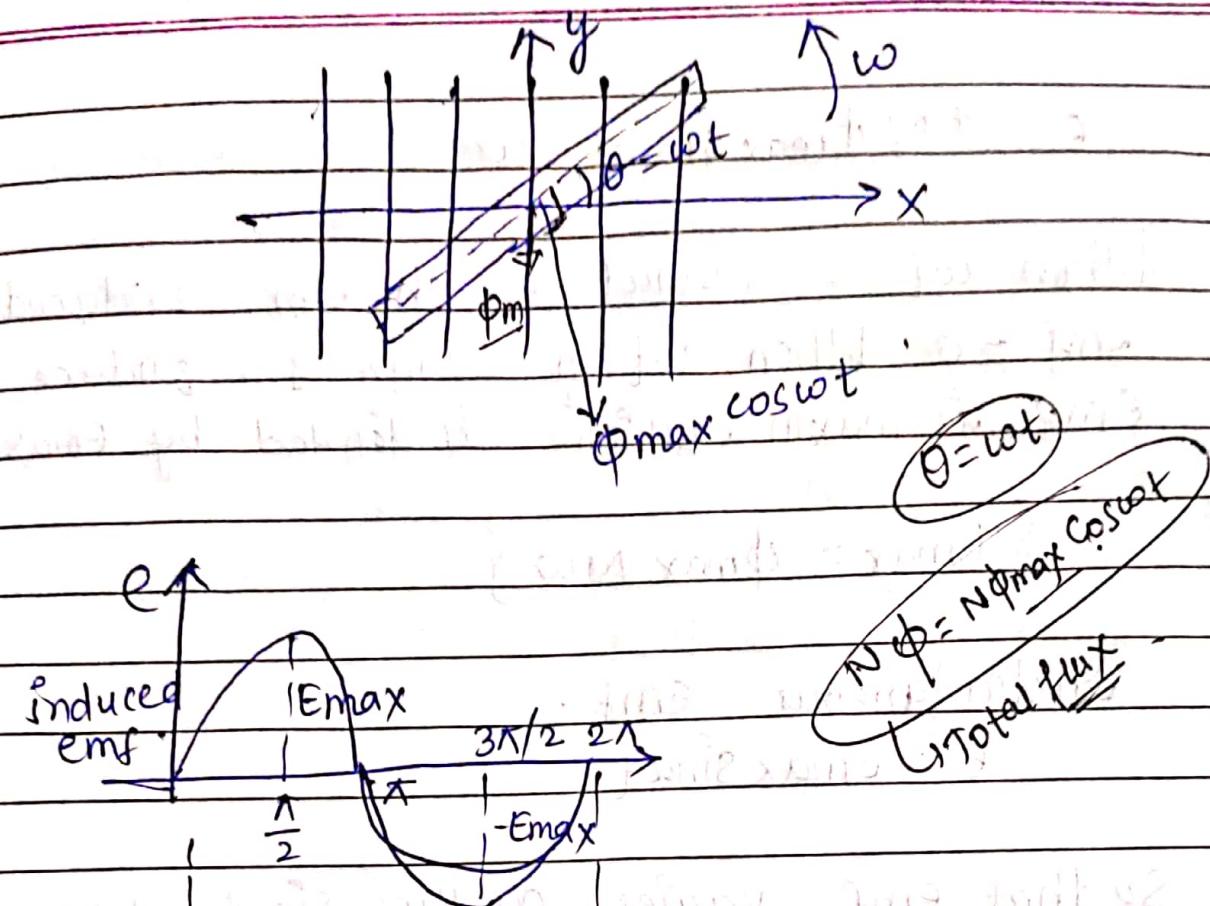

- The angle, θ through which the coil has rotated in "t" seconds = ωt
- In this position the component of flux along perpendicular to the plane of coil = $\phi_{\text{max}} \cos \omega t$
- Hence ϕ linkage of the coil at this instant is equal to {No. of turns on coil \times Linking flux} that is instant flux linkage = $N \phi_{\text{max}} \cos \omega t$. According to Faraday's law of Electromagnetic induction.
- Emf induced in a coil = Rate of change of flux linkage with -ve sign.

$$e = -\frac{d}{dt} (N \phi_{\text{max}} \cos \omega t)$$

$$e = +N \phi_{\max} \sin \omega t \cdot \omega$$

When $\omega t = 0$, $\sin \omega t = 0$, therefore induced emf = 0. When $\omega t = \frac{\pi}{2}$, $\sin \frac{\pi}{2} = 1$. Induced emf is maxm. which is denoted by E_{\max} .

$$\left\{ \begin{array}{l} E_{\max} = \phi_{\max} N \omega \\ e = E_{\max} \sin \omega t \end{array} \right.$$

Instantaneous emf.

$$e = E_{\max} \sin \omega t$$

So that emf varies as the sin function of the time varies with time. And if emf induced is plotted against time, A curve of sin wave shape is obtained. Such an emf is called sinusoidal emf. The sin wave is completed when the coil rotates through an angle of 2π radians.

• Reactance

This is the opposition in ohm offered by Inductance and capacitance in the circuit.
Inductive reactance $X_L = \omega L$ (n)

ω = angular frequency in rad/sec.
 $= 2\pi f$.

f = frequency in Hz or cycle/second.

• Capacitive reactance $X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$

• Impedance : Complex summation of Resistance and reactance. Its unit is Ω .

$$Z = R + jX$$

$$= R + j(X_L - X_C)$$

$$R + j(\omega L - \frac{1}{\omega C})$$

$$|Z| = \sqrt{R^2 + (X_L - X_C)^2}$$


$$|Z| = \sqrt{R^2 + X^2}$$

$$\angle Z = \phi = \tan^{-1}\left(\frac{X}{R}\right)$$

This is also the angle between voltage and current in the circuit and known as power factor angle.

• Different forms of emf equation
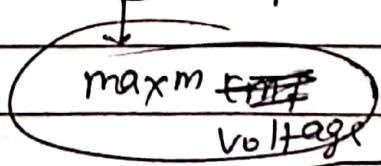
$$e = E_m \sin \theta = E_m \sin \omega t = (E_m) \sin \frac{2\pi}{T} t = E_m \sin 2\pi ft$$



$$I = I_m \sqrt{R^2 + 4\omega^2 L^2}$$


$$f = \omega / \pi$$

$$\left\{ I_{avg} = \frac{I_{max}}{\sqrt{2}} \right\}$$

- The RMS value of an alternating quantity is given by that steady (d.c) current which when flowing through a given circuit for given time produces the same heat as produced by the alternating current when flowing through the same circuit for the same time. Also known as effective or virtual value of AC.

* Impedance triangle.

$$|z| = \sqrt{R^2 + X^2}$$

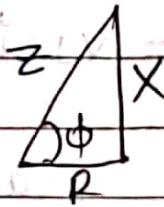

Admittance -

$$Y = \frac{1}{Z} = \frac{I}{V}$$

$$Y = G + jB$$

Conductance

Susceptance

reciprocal of reactance.

reciprocal of
Resistance.

Power:-

There are three types of power in Alternating circuit

i) Active power -

If it is the power which is actually consumed in the circuit or in resistor then

$$P = VI \cos \phi = I^2 R$$

It is also known as real power or true power.

ii) Reactive power:- It is the power taken by the reactance of the circuit. Its unit is Volt Amp-reactive (VAR).

It is denoted by Φ .
 $\Phi = VI \sin \phi = I^2 X$

Where X = Reactance in ohm.

(iii) Apparent power - (S) -

It is given by the product of Rms value of voltage and current. Its unit is Volt-amp (VA) and is given by

$$S = VI = I^2 Z$$

$$Z = \text{Impedance}$$

- $S = P + j\Phi \rightarrow \text{Relation.}$

$$\begin{array}{c} S = I^2 Z \\ \angle \Phi \\ P = I^2 R \end{array}$$

$$S = \sqrt{P^2 + Q^2}$$

$$\Phi = \tan^{-1}\left(\frac{Q}{P}\right)$$

- Power factor - It is the cosine of the angle b/w voltage & current.


$$P.f = \cos\phi = \frac{R}{Z}$$

$$P.f = \frac{P}{S} = \frac{R}{Z}$$

- Phasor diagram:

$$\vec{V} = |V| \angle 0^\circ$$

$$\vec{I} = |I| \angle \phi$$

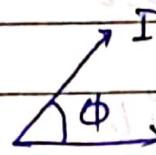


i) \rightarrow Voltage is reference and current is leading by an angle ϕ

ii) \rightarrow Voltage is reference & current is lagging by an angle ϕ .

$$\vec{V} = |V| \angle 0^\circ$$


$$\vec{I} = |I| \angle -\phi$$

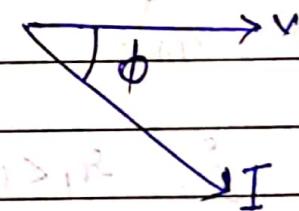

iii) Voltage is not reference but current is leading by an angle ϕ .


$$\vec{V} = |V| \angle \theta$$

$$\vec{I} = |I| \angle \theta + \phi$$

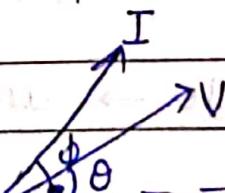

reference line.

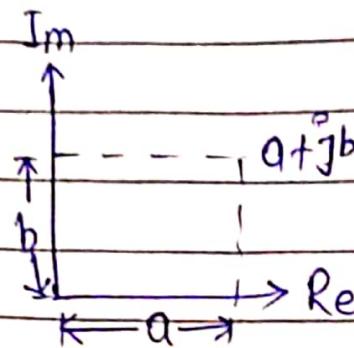Complex representation of Voltage & current



Rectangular or Cartesian representation.

$$i = a + jb$$

$$\vartheta = c + jd$$

Where $j = \sqrt{-1}$ which gives the rotation through 90° in anticlockwise direction.


a = Real part b = Imaginary part

X-axis - real axis

Y-axis - Imaginary axis.

$$i = r_1 \angle 0,$$

$$v = r_2 \angle \vartheta_2$$

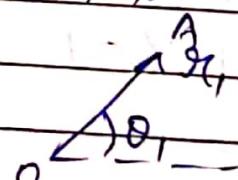

Properties of Operator j

$j = 90^\circ \rightarrow$ anticlockwise rotation of a phasor


$$= \sqrt{-1}$$

$j^2 = 180^\circ \rightarrow$ anticlockwise rotation of a phasor

$$= -1$$

$j^3 = 270^\circ \rightarrow$ anticlockwise rotation of a phasor

$$= -j$$

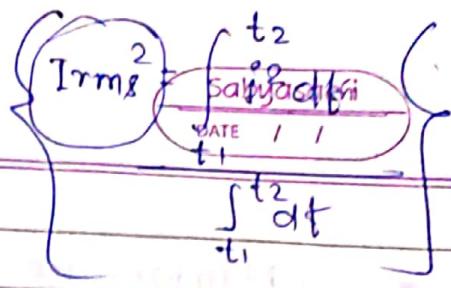

$$\frac{1}{j} = -j.$$

* RMS and Avg. value:

RMS / effective value

Root mean square value

$$I_{rms} = \sqrt{\text{average } i^2(t)} \quad \text{Mid ordinate method}$$

$$= \sqrt{\left(\frac{i_1^2 + i_2^2 + i_3^2 + \dots + i_n^2}{n} \right)} \quad n \rightarrow \text{Complete cycle.}$$

Square root of the mean of the square of the instantaneous current over one cycle.

$$I_{av} = \frac{i_1 + i_2 + \dots + i_n}{n}$$

over the half cycle

$$i = I_m \cos \omega t = I_m \cos \frac{2\pi}{T} t$$

$$I_{rms} = \left[\frac{1}{T} \int_0^T i^2 dt \right]^{1/2} \quad \text{Analytical method.}$$

\Rightarrow RMS current.

- Instantaneous power dissipation in a resistor is

$$\{ P = i^2 R \}$$

- Avg. power dissipation over one half cycle

$$\{ P = \frac{1}{T} \int_0^T i^2 R dt \}$$

$$P = i^2 R$$

$$\text{Where } I = I_{\text{rms}} = \left[\frac{1}{T} \int_0^T i^2 dt \right]^{1/2}$$

Rms current

Consider an AC of sinusoidal current

$$i = I_m \cos \omega t$$

$$I_{\text{rms}} = \left[\frac{1}{T} \int_0^T I_m^2 \cos^2 \omega t dt \right]^{1/2}$$

$$I_{\text{rms}} = \left[\frac{1}{T} \int_0^T I_m^2 \left(\frac{1 + \cos 2\omega t}{2} \right) dt \right]^{1/2}$$

$$\left[\frac{1}{T} \left(\frac{I_m^2}{2} t + \frac{\sin 2\omega t}{2\omega} \right) \right]_0^T$$

$$\left[\frac{1}{T} \left(I_m^2 t + \frac{\sin 4\omega T}{4\omega} \right) \right]^{1/2}$$

$$I_{rms}^2 = \frac{1}{T} \left[I_m^2 T + \frac{\sin 4\pi XT}{2} \right] = 0 - 0$$

$$I_{rms} = \frac{I_m^2}{\sqrt{2}} + \frac{\sin 4\pi XT}{2} = \frac{I_m}{\sqrt{2}}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$I_{avg} = \frac{1}{T} \int_0^T I_m \cos \frac{4\pi t}{T} dt$$

$$\begin{aligned} I_{avg} &= \frac{1}{T} \int_0^T \left(I_m \left(1 + \cos \frac{4\pi t}{T} \right) \right) dt \\ &= \frac{I_m}{2} \left(t + \frac{\sin \frac{4\pi t}{T}}{\frac{4\pi}{T}} \right) \Big|_0^T \end{aligned}$$

$$I_{avg} = \frac{I_m}{2} \left[T + \frac{1}{4\pi} \sin \frac{4\pi T}{T} \right]$$

$$I_{avg} = \frac{1}{T} \int_0^T I_m \cos \omega t dt$$

$$I_{avg} = \frac{1}{T} \cdot I_m \cdot \left[\frac{\sin \omega t}{\omega} \right]_0^T$$

$$\frac{1}{T} I_m \cdot \left[\frac{\sin \omega T}{\omega} - \sin 0 \right]$$

$$\frac{\omega}{2\pi} \times \frac{I_m}{\omega} \times \sin \frac{\omega \times 2\pi}{\omega}$$

$$I_{avg} = \frac{1}{T} \int_0^{\pi/\omega} I_m \sin \omega t dt$$

$$I_{avg} = \frac{I_m}{\omega} \left[\sin \omega t \right]_0^{\pi/\omega}$$

$$I_{avg} = \frac{I_m}{\omega} \left[\frac{\sin \frac{\pi}{\omega} \times \omega}{\omega} \right]_0^{\pi/\omega} \Rightarrow \frac{I_m}{\omega} \times 0 = 0$$

$$\left\{ \begin{array}{l} I_{avg} = \frac{1}{T} \int_0^T i dt \\ I_{rms} = \left[\frac{1}{T} \int_0^{T/2} i^2 dt \right]^{1/2} \end{array} \right.$$

~~# problem~~ Q. 1 Find rms and avg value of the output of half wave rectifier



$$i_m = I_m \sin \omega t$$

$$T = 2\pi$$

$$I_{rms}^2 = \frac{1}{2\pi} \left[\int_0^{\pi} i^2 d(\omega t) + \int_{\pi}^{2\pi} 0 d(\omega t) \right]$$

$$I_{rms}^2 = \frac{1}{2\pi} \left[\int_0^{\pi} I_m^2 \sin^2 \omega t d(\omega t) \right]$$

~~$$\frac{1}{2\pi} \int_0^{\pi} \cos^2 \omega t d(\omega t)$$~~

~~$$\frac{1}{2\pi} \int_0^{\pi} \cos^2 \omega t d(\omega t)$$~~

$$\frac{1}{2\pi} \int_0^{\pi} I_m^2 \left(\frac{1 + \cos 2\omega t}{2} \right) d(\omega t)$$

$$\frac{1}{2\pi} \frac{I_m^2}{2} \left(\frac{1}{2} \omega t - \frac{\sin 2\omega t}{2} \right) \Big|_0^{\pi}$$

$$\frac{1}{4\pi} I_m^2 \left(\frac{\omega t \pi}{2} - \frac{\sin 2\pi}{2} \right)$$

~~$$I_{rms}^2 = \frac{I_m^2}{4\pi} \times \cancel{\pi}$$~~

$$I_{rms} = \frac{I_m}{2} = 0.5 I_m$$

$$I_{avg} = \frac{1}{2\pi} \int_0^{\pi} i d(\omega t)$$


$$\frac{1}{2\pi} \int_0^{\pi} I_m \sin \omega t d(\omega t)$$

$$\frac{1}{2\pi} I_m \cdot (-\cos \omega t) \Big|_0^{\pi}$$

$$(-\frac{1}{2\pi} \times I_m (-1) - 1) = \frac{I_m}{\pi}$$


Q. 2 Find the power factor and peak factor for the above half wave rectifier.

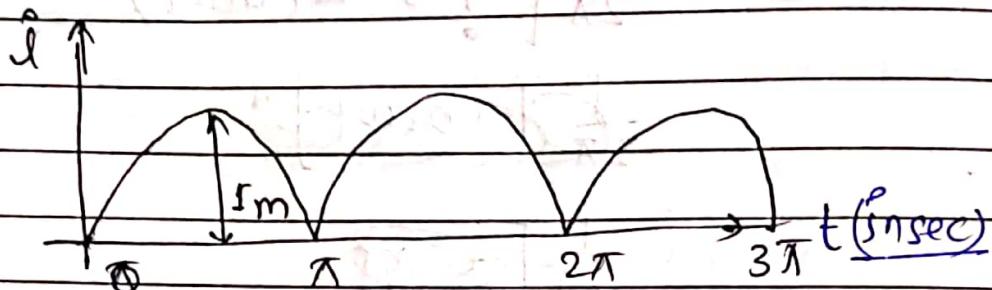Q. 3 For the output of full wave rectifier determine A) RMS value B) Avg value C) form factor d) peak factor.



Q. 4 For the saw tooth wave.


Determine the form factor.

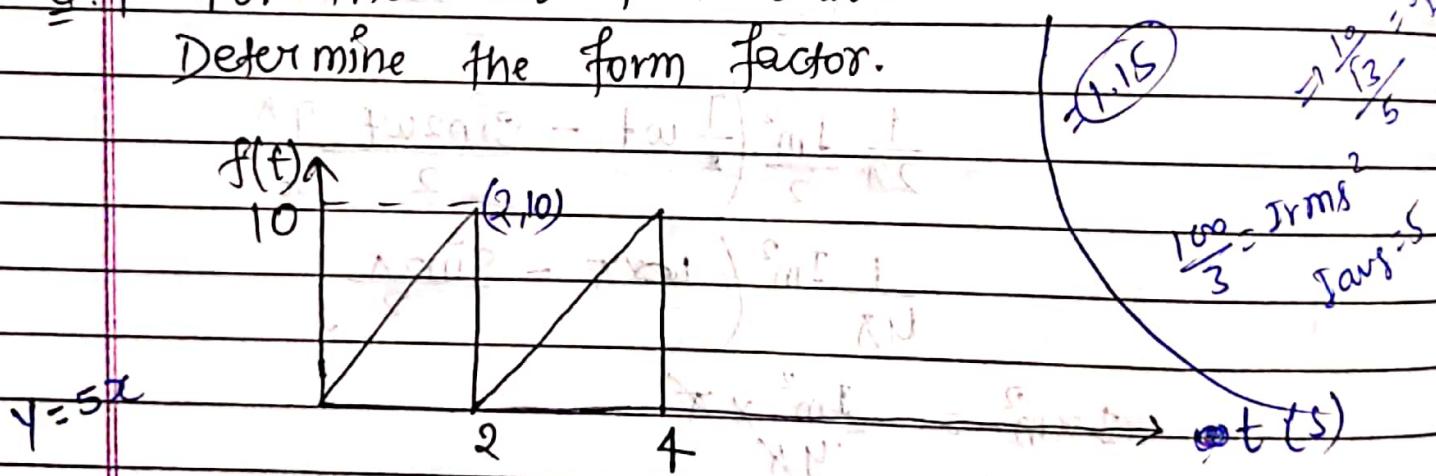

Q. 5 Find the effective or RMS value for the voltage function.

$$V(t) = 20 + 30 \sin \omega t + 60 \sin(2\omega t - \pi/2) -$$

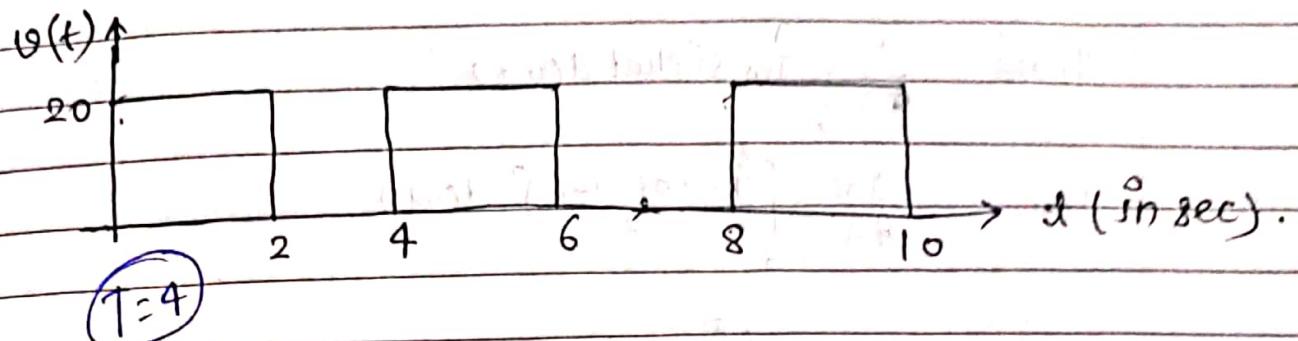Q. 6 Find the RMS value, Avg value, form factor and peak factor for the pulse train shown in figure.



- Q7 An AC circuit has frequency 50Hz and RMS current 25A. Write equation of and find current at time 0.0025 sec. Time at b) Time at which current 14.14 Amp.

$$i = I_m \sin(\omega t + \phi_0)$$

form factor = $\frac{I_{rm}}{I_{avg}} = \frac{\pi}{2\sqrt{2}} = 1.11$

power factor = $\frac{I_m}{I_{rm}} = \sqrt{2}$

Soln (2) form factor = $0.5 I_m \times \pi = 0.5 \pi = 1.57$

power factor = $\frac{I_m}{0.5 I_m} = 2$

Soln (3) $i = I_m \sin^2 \omega t$

$$I_{avg} = \frac{1}{T} \int_0^T I_m \sin^2 \omega t d(\omega t) \quad \left(I_{avg} = \frac{I_m}{2} \right)$$

$$\frac{I_m}{T} \int_0^T \frac{1 - \cos 2\omega t}{2} d(\omega t)$$

$$\frac{I_m}{T} \times \left[\frac{\omega t - \frac{\sin 2\omega t}{2\omega} \Big|_0^T}{2\omega} \right] \Rightarrow \frac{I_m}{4\pi} \times \pi = \frac{I_m}{4} \times I_{rm} = \frac{I_m}{2}$$

$$a) I = 25\sqrt{2} \sin 100\pi t \times 0.0025$$

$I_{\text{rms}} = 25A$

$$I = 25\sqrt{2} \sin \frac{\pi}{50} = 25\sqrt{2} \times \frac{1}{\sqrt{2}} = 25A$$

$I_m = \sqrt{2} \times 25 = 35.35A$
 $\vec{I} = I_m \sin \omega t$

$$b) 14.14 = 25\sqrt{2} \sin 100\pi t$$

$35.35 \sin 314t$

$$14.14 = 25 \times 1.41 \sin 100\pi t$$

$$i = 35.35 \sin 314t$$

~~radian~~


$$\frac{\pi}{180} \times \frac{23.6}{100\pi} = t$$

$$t = 0.075 \text{ sec}$$

$$t = 0.0013 \text{ sec.}$$

Soln.

(3)

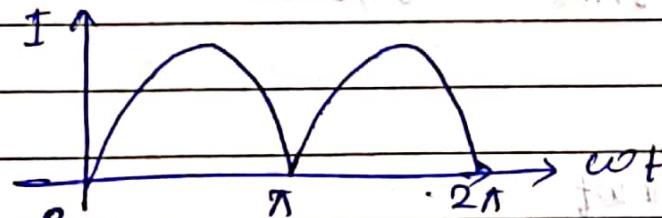

$$\text{Time period} = \pi$$

$$I_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T i^2 dt}$$

$$\sqrt{\frac{1}{\pi} \int_0^\pi I_m^2 \sin^2 \omega t d(\omega t)}$$

$$\sqrt{\frac{I_m^2}{2\pi} \int_0^\pi (1 - \cos 2\omega t) d(\omega t)}$$

$$\frac{I_m}{\sqrt{2}} = 0.707 I_m$$

Arg value

$$I_{\text{avg}} = \frac{1}{T} \int_0^T I_m \sin \omega t dt$$

$$I_{avg} = \frac{1}{\pi} \int_0^{\pi} I_m \sin \omega t d(\omega t)$$

$$\frac{I_m}{\pi} \left[-\cos \omega t \right]_0^{\pi}$$

$$-\frac{I_m}{\pi} [-1 - 1] = \frac{2I_m}{\pi}$$

$$I_{avg} = 0.637 \underline{I_m}$$

$$\text{Form factor} = \frac{I_{rms}}{I_{avg}} = \frac{0.707 \underline{I_m}}{0.637 \underline{I_m}}$$

$$\text{Peak factor} = \frac{I_m}{I_{rms}} = \frac{I_m}{0.707 \underline{I_m}} =$$

Soln

$$(5) v(t) = 20 + 30 \sin \omega t$$

$$\text{Soln} (4) I_{rms}^2 = \frac{1}{2} \int_0^2 (5t)^2 dt$$

$$f(t) = 5t$$

$$I_{rms}^2 = \frac{1}{2} \left[\frac{25t^2}{3} \right]_0^2 = I_{rms}^2 = \frac{1}{2} \times 25 \left[\frac{4}{3} \right]$$

$$I_{rms} = \frac{50}{3} = \frac{50}{\sqrt{3}}$$

$$I_{avg} = \frac{1}{2} \int_0^2 s dt$$

$$\frac{1}{2} \left(\frac{5t^2}{2} \right)_0^2 = \frac{1}{2} \left[5 \times \frac{4}{2} \right] = 5$$

~~Form factor~~

$$\text{Form factor} = \frac{5}{\frac{50}{\sqrt{3}}} = \frac{10}{10} = \frac{2}{\sqrt{3}} = 1.1$$

$$V(t) = 20 + 30 \sin \omega t + 60 \sin(2\omega t - \frac{\pi}{2})$$

Soln:
⑤

$$V_{rms}^2 = \frac{1}{T} \int_0^T V^2 dt$$

$$V_{rms}^2 = \frac{1}{2\pi} \int_0^{2\pi}$$

$$V_{rms}^2 = \sqrt{(20)^2 + \left(\frac{30}{\sqrt{2}}\right)^2 + \left(\frac{60}{\sqrt{2}}\right)^2}$$

$$I = I_m \sin \omega t$$

$$(I_{rms} = \frac{I_m}{\sqrt{2}})$$

$$\sqrt{400 + 450 + 1800} \\ = 51.478 V.$$

$$⑥ V_{rms}^2 = \frac{1}{T} \int_0^T V^2 dt$$

$$V_{rms}^2 = \frac{1}{4} \int_0^2 (20)^2 dt + \frac{1}{4} \int_2^4 0 dt$$

$$V_{rms}^2 = \frac{1}{4} \left[\frac{40^3}{3} \right]_0^2 = \frac{1}{4} \times \frac{8}{3} = \frac{2}{3}$$

$$V_{rms} = \frac{P}{\sqrt{3}}$$


$$V_{rms} = \frac{1}{4} \int_0^2 V^2 dt \\ \frac{1}{4} \times 40 = 10$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$\text{Form factor} = 1.414$$

$$\text{Peak factor} = 1.414$$


- Ac through pure resistive circuit :-

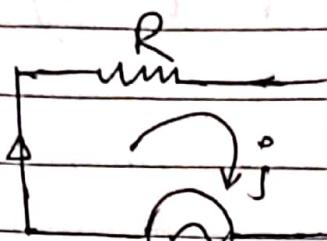

$$V = V_m \sin \omega t$$

$$\{ I = \frac{V}{R} = \frac{V_m \sin \omega t}{R} = \frac{I_m \sin \omega t}{R}$$

$$V = V_m \sin \omega t$$

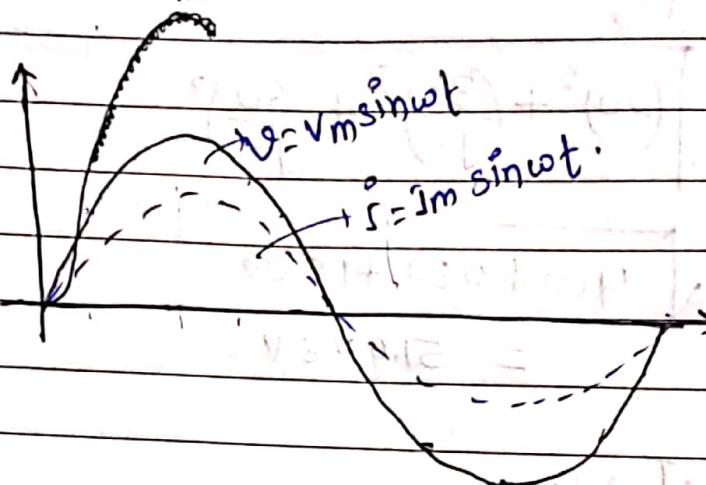

$$P.F. = \cos \phi$$

$$\phi = 0$$

$$P.F. = \cos 0 = 1$$

- power - instantaneous power.

$$P = VI$$

$$= V_m \sin \omega t \cdot I_m \sin \omega t$$

$$V_m I_m \sin^2 \omega t$$

$$\frac{V_m I_m}{2} (1 - \cos 2\omega t)$$

$$P = \frac{V_m I_m}{2} - \frac{V_m I_m}{2} \cos 2\omega t$$


power consists of a constant part $\frac{V_m I_m}{2}$ and a fluctuating part $\frac{V_m I_m \cos 2\omega t}{2}$

frequency double that of voltage and current waves. for a complete cycle
The average value of $\frac{V_m I_m \cos 2\omega t}{2} = 0$
Hence power for the whole cycle is .

$$\{ P = \frac{I_m V_m}{2} = \frac{V_m \times I_m}{\sqrt{2} \times \frac{T}{2}} = V_{rms} \times I_{rms} = V I \}$$


$V = \text{rms value of applied voltage}$

$I = \text{rms value of the current}$

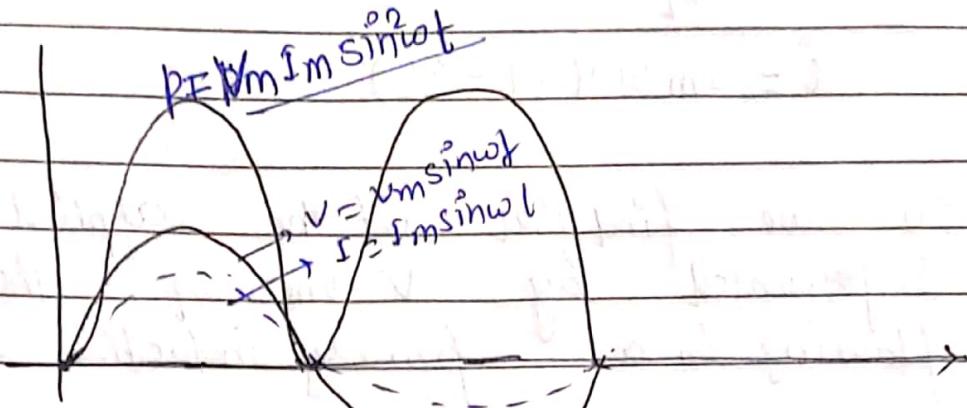

$$\left. \begin{aligned} V &= V_m \sin \omega t \\ I &= I_m \sin \omega t \end{aligned} \right\} P.E. = V_m I_m \sin^2 \omega t$$

Ac through pure inductive circuit.

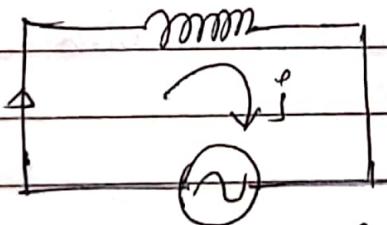

$$V = V_m \sin \omega t$$

$$V = L \frac{di}{dt}$$

$$V_m \sin \omega t = L \frac{di}{dt}$$

$$\int di = \frac{V_m}{L} \int \sin \omega t dt$$

$$i = \frac{V_m}{L} \left[-\frac{\cos \omega t}{\omega} \right]$$

$$i = \frac{V_m}{\omega L} \sin \left(\omega t - \frac{\pi}{2} \right)$$

$$\left. \begin{aligned} i &= \frac{V_m}{\omega L} \sin \left(\omega t - \frac{\pi}{2} \right) \end{aligned} \right\}$$

Maximum value of i is:


$$I_m = \frac{V_m}{X_L} \text{ when } \sin(\omega t - \frac{\pi}{2}) \text{ is unity}$$

$$i = I_m \sin(\omega t - \frac{\pi}{2})$$

So we find that if the applied voltage is represented by $V = V_m \sin \omega t$ then current flowing in a purely inductive circuit

$$= \left\{ i = I_m \sin(\omega t - \frac{\pi}{2}) \right\}$$

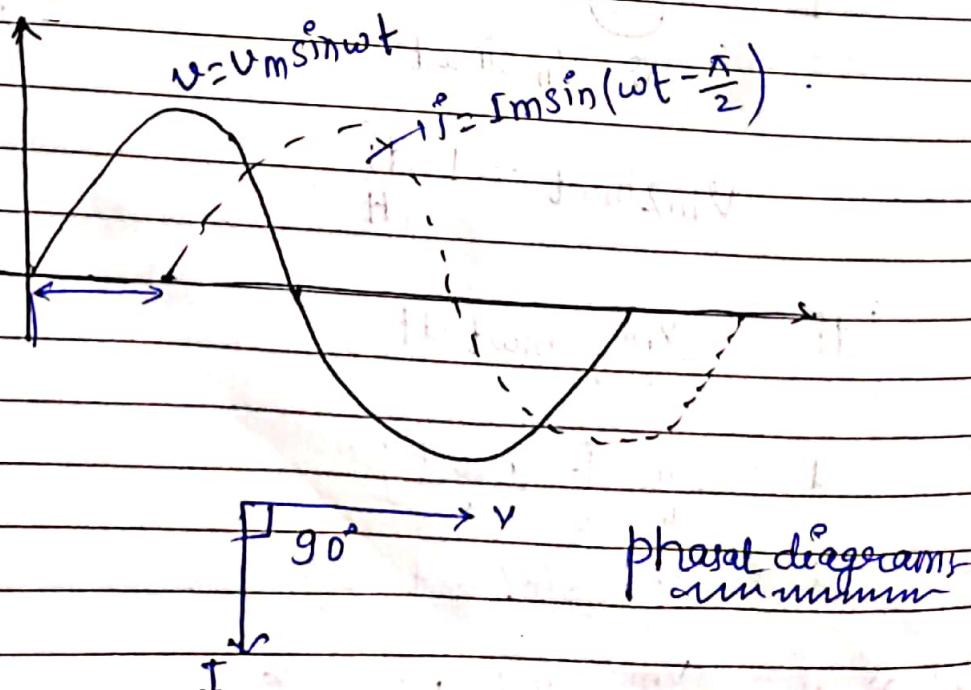Clearly the current lags behind the applied voltage by a quarter cycle or the phase difference between the two is $\frac{\pi}{2}$. (Voltage and current) with voltage leading.



Instantaneous power.

$$V = V_m \sin \omega t$$
$$i = I_m \sin(\omega t - \frac{\pi}{2})$$

$$p = V_m I_m \sin \omega t$$

$$= V_m I_m \sin \omega t \cos \omega t$$

$$p = -\frac{V_m I_m}{2} \sin 2\omega t$$


$$\text{power factor} = -\frac{V_m I_m}{2} \int_0^{2\pi} \sin 2\omega t dt$$
$$= 0$$

So the avg. power taken by the inductor for the complete cycle is zero.

$$\phi = 90^\circ \quad \{ \text{lagging} \}$$

$$P \cdot f = \cos \phi = \cos 90^\circ = 0$$

• AC circuit through pure Capacitor.

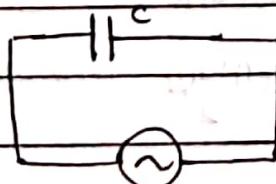

V = potential difference b/w plates at any instant.

q = charge on plates at that instant.

$$\text{Thus } q = CV$$

$$q = C V_m \sin \omega t$$

$$i = \frac{dq}{dt} = \frac{d}{dt} (V_m \sin \omega t)$$

$$= \omega C V_m \cos \omega t$$

$$i = \frac{V_m}{V_{AC}} \cos \omega t$$


$$i = \frac{V}{V_{AC}} \sin(\omega t + \frac{\pi}{2})$$

$$I_m = \frac{V_m}{c}$$

$$i = I_m \sin(\omega t + \frac{\pi}{2})$$

$$X_C = \frac{1}{\omega c}$$

= Capacitive Reactance (Ω)

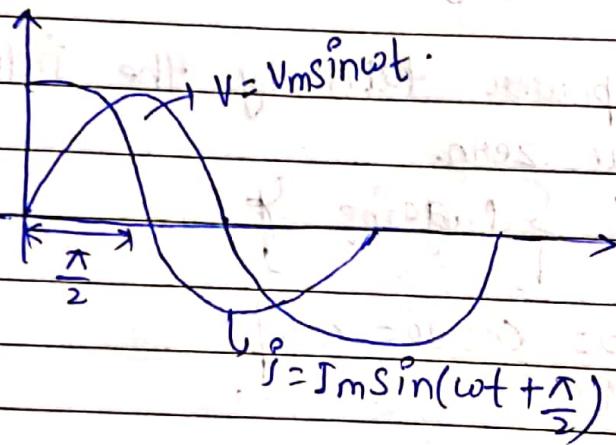


$$P = V_i i$$

$$= V_m \sin \omega t \cdot I_m \sin(\omega t + \frac{\pi}{2})$$

$$V_m I_m \sin \omega t \cos \omega t$$
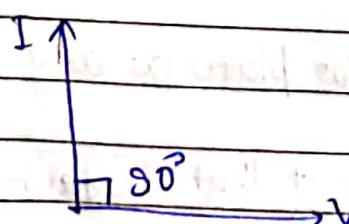
$$\{ \phi = \frac{V_m I_m}{2} \sin \omega t \}$$



power for the whole cycle =

$$\frac{1}{2} V_m I_m \int_0^{2\pi} \sin^2 \omega t dt = 0$$


\Rightarrow Power factor = Angle b/w voltage and current

$$\phi = 90^\circ \text{ leading } PF = \cos \phi = \cos 90^\circ = 0$$

(Leading)

* AC through resistive inductive circuit.

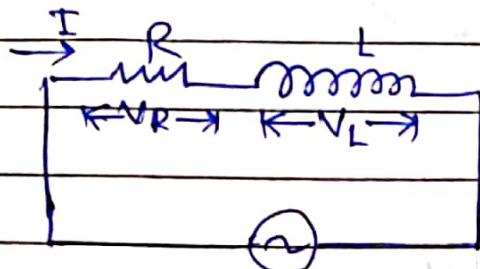let $V = \text{Rms value of one applied voltage}$.
 $I = \text{Rms value of one resistive current}$.



$V_R = IR = \text{Voltage drop across } R$.

$V_L = IX_L = \text{Voltage drop across coil}$

Total impedance of one circuit.

$$Z = R + jX_L = R + j\omega L$$

$$I = \frac{V}{Z} = \frac{V_m \sin \omega t}{\sqrt{R^2 + X_L^2}} \quad \tan^{-1}\left(\frac{X_L}{R}\right)$$

$$= \frac{V_m}{\sqrt{R^2 + X_L^2}} \sin\left(\omega t - \tan^{-1}\left(\frac{X_L}{R}\right)\right)$$

$$= \frac{V_m}{\sqrt{R^2 + X_L^2}} \sin(\omega t - \phi)$$



$$I = I_m \sin(\omega t + \phi)$$

$I_m = \text{max value of current}$.

$$\frac{V_m}{\sqrt{R^2 + X_L^2}}$$

$\phi = \text{Angle b/w voltage & current}$.
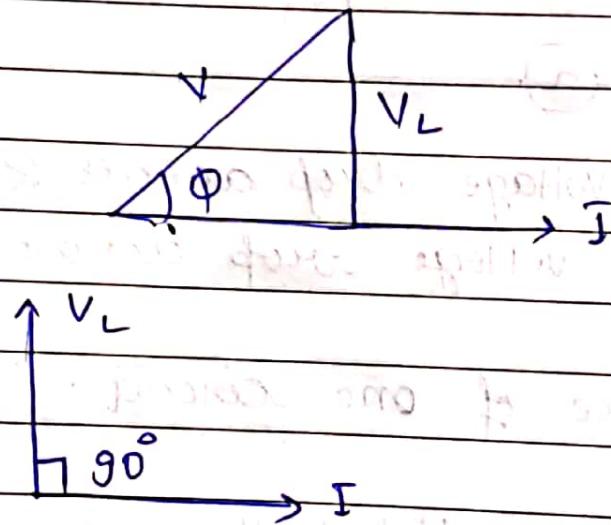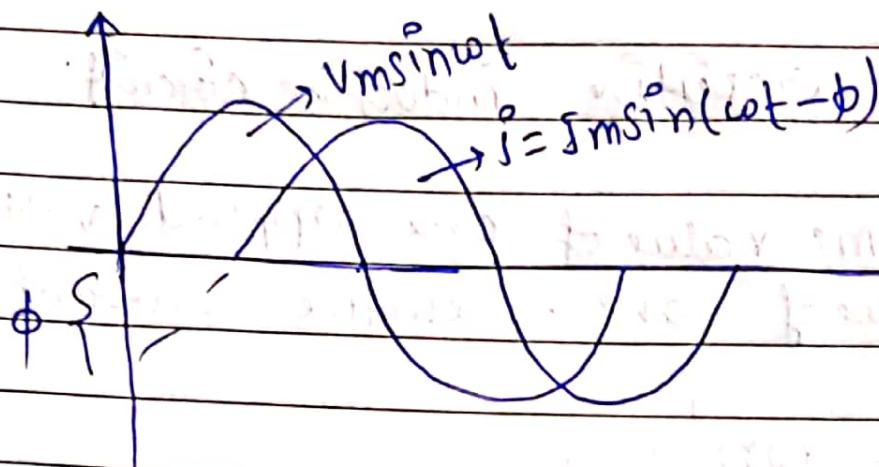
$$\phi = \tan^{-1} \frac{X_L}{R} = \tan^{-1} \left(\frac{\omega L}{R} \right).$$



power \Rightarrow Active power

$$P = VI \cos \phi$$

V_m forms $\cos \phi$


$$P = VI \cos \phi$$

$$VI \frac{R}{Z} = \frac{V}{Z} IR$$

$$\{ P = I^2 R \}$$

$$\text{power factor} = \phi = \tan^{-1} \frac{X_L}{R} = \tan^{-1} \left(\frac{\omega L}{R} \right)$$

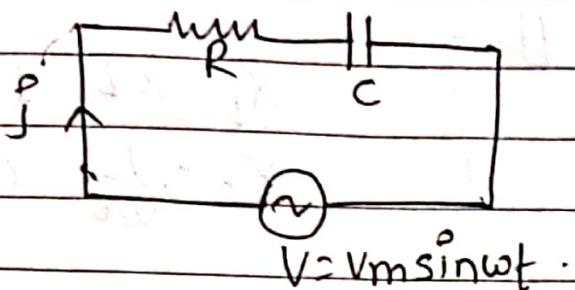AC through Resistive and Capacitive circuit.




$$X_L = \frac{1}{\omega C} \quad z = R - jX_C = R - \frac{j}{\omega C}$$

polar form $\Rightarrow z = \sqrt{R^2 + X_C^2} \angle \tan^{-1}\left(\frac{X_C}{R}\right)$.

$$i = \frac{V}{z} = \frac{V_m \sin \omega t}{\sqrt{R^2 + X_C^2}} \angle \tan^{-1}\left(\frac{X_C}{R}\right)$$

$$I_m = \frac{V_m}{\sqrt{R^2 + X_C^2}}$$

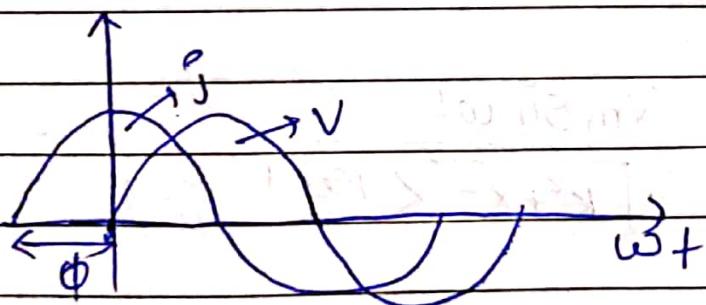
$$\phi = \tan^{-1}\left(\frac{X_C}{R}\right) = \tan^{-1}\left(\frac{1}{\omega C R}\right)$$



Average power is consumed by one zero so the power consume by active power.

$$\text{power factor angle } \phi = \tan^{-1}\left(\frac{X_C}{R}\right)$$

A-C through Series R-L-C Circuit.

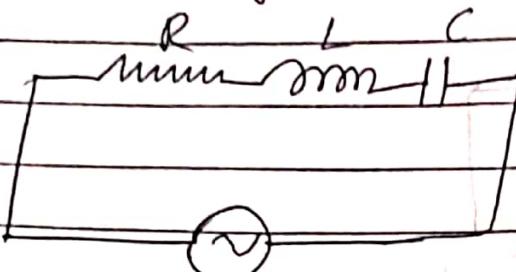

$$X_L = \omega L \quad \text{Inductive Reactance}$$

$$X_C = \frac{1}{\omega C} \quad \text{Capacitive Reactance}$$

$$V = V_m \sin \omega t$$

$$Z = R + j(X_L - X_C)$$

$$R + j(\omega L - \frac{1}{\omega C})$$

In polar form:

$$Z = \sqrt{R^2 + x^2} \angle \tan^{-1} \frac{x}{R}$$

$$x = X_L - X_C$$

The resultant current I in the circuit.

$$I = \frac{V}{Z} = \frac{V_m \sin \omega t}{\sqrt{R^2 + x^2} \angle + \tan^{-1} \left(\frac{x}{R} \right)}$$

$$I = \frac{V_m \sin \omega t}{\sqrt{R^2 + x^2}} \left(\omega t - \tan^{-1} \frac{x}{R} \right)$$

Now there are two cases

$$\text{i) } X_L > X_C \text{ or } V_L > V_C$$

V_L = voltage across the inductor

V_C = voltage across the capacitor

$$\textcircled{1} \Rightarrow V = iX_c.$$

In this case the circuit is inductive.

$$\phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right) \text{ angle of lag}$$


$$(ii) X_C > X_L \quad \text{or} \quad U_C > U_L.$$

In this case nature of circuit is capacitive.
Capacitive current i leads the voltage by angle ϕ .

$$\phi = \tan^{-1} \left(\frac{X_C - X_L}{R} \right) \text{ angle of lead.}$$

Series and parallel AC circuit


series

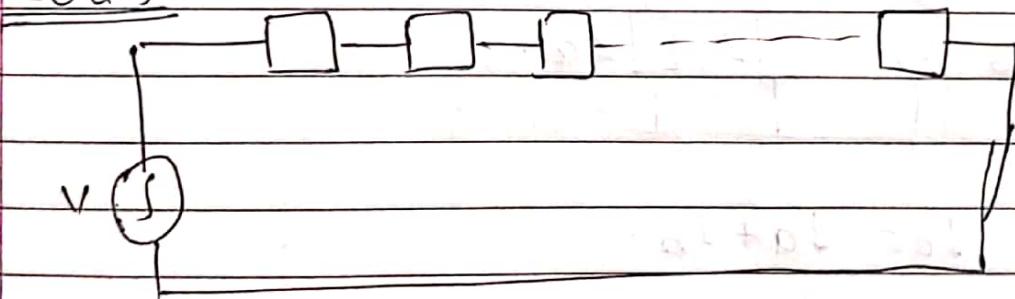

$$V = IZ_1 + IZ_2 + \dots + IZ_n = IZ_{eq}.$$

$$Z_{eq} = Z_1 + Z_2 + \dots + Z_n.$$

parallel

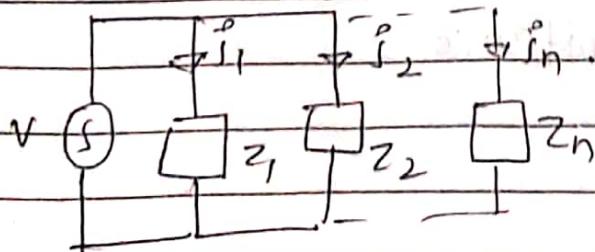

$$I = \frac{V}{Z_1} = VY_1, \quad I = \frac{V}{Z_2} = VY_2$$


$$I = I_1 + I_2 + \dots + I_n$$

$$VY_{eq} = VY_1 + V_2 + \dots + VY_n.$$

$$VY_{eq} = V(Y_1 + Y_2 + \dots + Y_n)$$

$$Y_{eq} = Y_1 + Y_2 + \dots + Y_n.$$

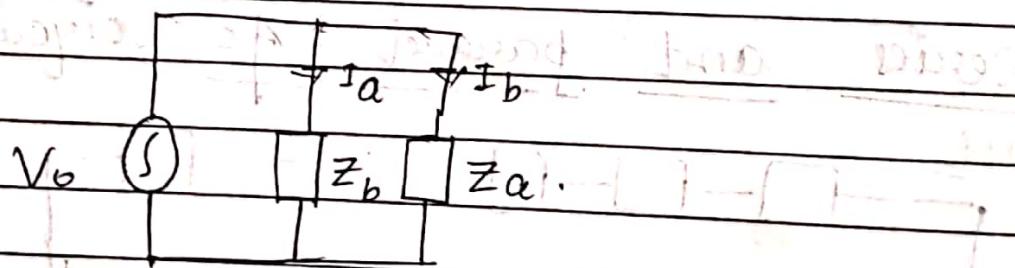• Current and voltage division in a.c circuit.



$$I_o = I_a + I_b.$$

$$I_a = \frac{I_o \times Z_b}{Z_a + Z_b} = \frac{Y_a}{Y_a + Y_b} I_o$$


$$I_b = \frac{I_o Z_a}{Z_a + Z_b} = \frac{Y_b}{Y_a + Y_b} Z_o$$

$\gamma \rightarrow$ Admittance.

$$V_b = I_o Z_b = \frac{Z_b V_o}{Z_a + Z_b} = \frac{Y_b}{Y_a + Y_b} V_o.$$

$$V_a = I_o Z_a = \frac{Z_a V_o}{Z_a + Z_b} = \frac{Y_a}{Y_a + Y_b} V_o$$


$$I_o = \frac{V_o}{Z_a + Z_b}$$

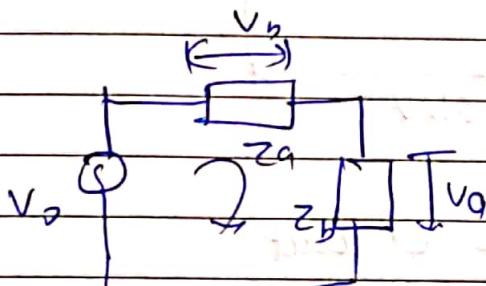

Quality factor = $\frac{1}{\cos \phi}$

- Q.1 In series R-L circuit shown in figure
 find a) Impedance b) Resultant current
 c) Power factor, nature d) Quality factor


Given $L = 0.1 H$.

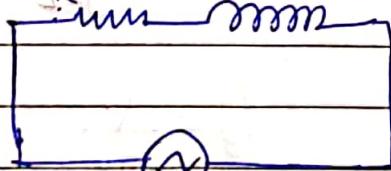

$220 < 0^\circ, 50 Hz$


In the given circuit find Active, reactive and Apparent power.

$R = 15 \Omega \quad L = 0.2 H$

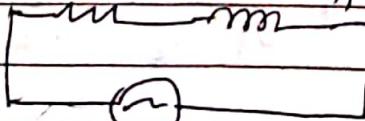

$220 < 0^\circ, 60 Hz$

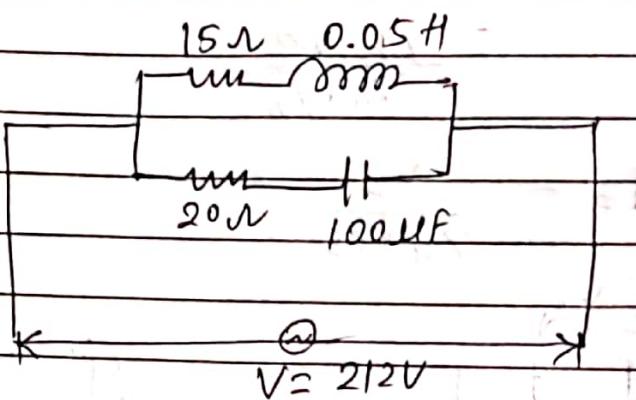Q.2 Determine the Rms value of current in each branch and total current of the circuit shown in figure.
Draw the phasor diagram.



* parallel R-L-C circuit

$$i_1 = \frac{V}{R}$$

$$i_2 = \frac{V}{jX_L} = \frac{V}{X_L} \angle -90^\circ$$

$$i_3 = \frac{V}{jX_C} = \frac{V}{X_C} \angle 90^\circ$$

$$i = i_1 + i_2 + i_3 \quad (\text{KCL})$$

$$\frac{1}{Z} = \frac{1}{R} + \frac{1}{jX_L} + \frac{1}{-jX_C}$$

$$\frac{1}{R} + j\left(\frac{1}{X_C} - \frac{1}{X_L}\right)$$

B

Admittance

$$y = \frac{1}{R} + j\left\{\frac{1}{X_C} - \frac{1}{X_L}\right\} = \frac{1}{Z}$$


$$G + jB$$

$$\frac{1}{R}$$

$$\frac{1}{X_C} - \frac{1}{X_L}$$

$B \rightarrow \text{susceptance}$

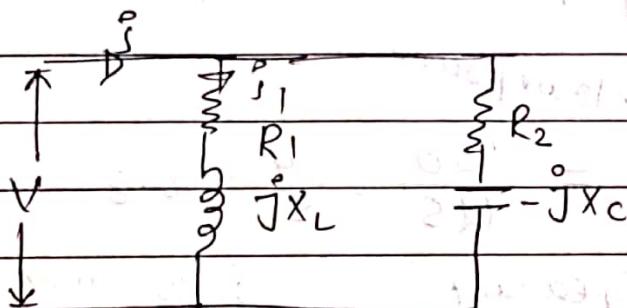- parallel Combination of Inductive & Capacitive Impedance.



$Z_1 = R_1 + jX_L$ = Impedance of Inductive branch.


$Z_2 = R_2 - jX_C$ = Impedance of Capacitive branch

$$\left\{ \begin{array}{l} I_1 = \frac{V}{Z_1} = \frac{V}{R_1 + jX_L} \\ I_2 = \frac{V}{Z_2} = \frac{V}{R_2 - jX_C} \end{array} \right\}$$

$$I = I_1 + I_2 = \frac{V}{R_1 + jX_L} + \frac{V}{R_2 - jX_C}$$

$$Y = Y_1 + Y_2$$
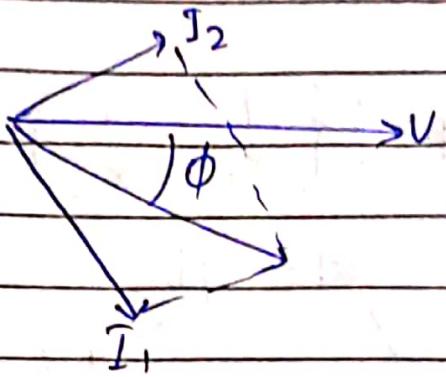
$$\frac{1}{Z_1} + \frac{1}{Z_2} = \frac{1}{R_1 + jX_L} + \frac{1}{R_2 - jX_C}$$




Importance of power factor.

A steel stamping operation runs at 100 kW (working power / true power) & the apparent

$$\cos \phi = \frac{T_p}{A_p} = \frac{100}{125} = \frac{4}{5} = 0.8$$


True power
Apparent power in % = 80%.

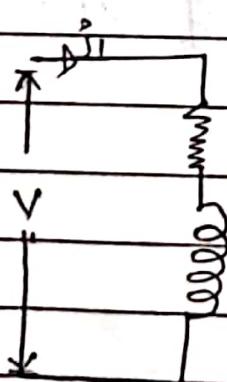Power factor correction by static capacitor.




ϕ_1

ϕ_1 = original phase angle.

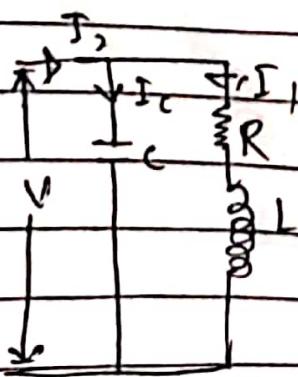

$$I_2 = I_1 + I_C$$

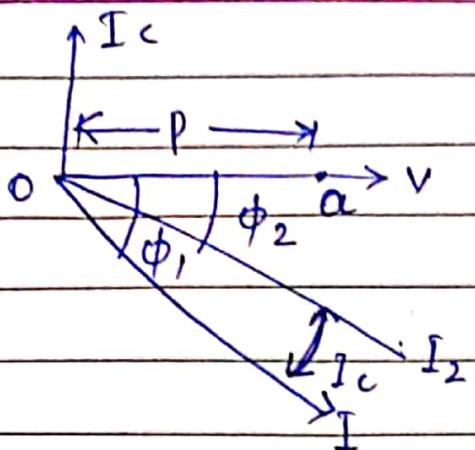

$$O \cdot a = I_1 \cos \phi_1 = I_2 \cos \phi_2 \quad \cos \phi_2 > \cos \phi_1, \\ I_2 < I_1,$$

It means that the current I_2 drawn from the supply is less than the load current I_1 , thereby reducing system loss & improve efficiency as well. From this since

$$\boxed{VI_2 \cos \phi_2 = VI_1 \cos \phi_1}$$

real power taken from the supply remains the same.

$$I_c = I_1 \sin \phi_1 = I_2 \sin \phi_2$$

$$V_c = VI_1 \sin \phi_1 - VI_2 \sin \phi_2$$

$$P = VI_1 \cos \phi_1 = VI_2 \cos \phi_2$$

we can write

$$\Phi_c = P(\tan \phi_1, -\tan \phi_2)$$

$$\Phi_c = VI_c$$